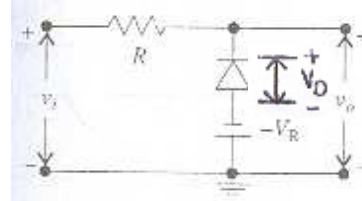


**negative peak or positive base clipper:**

Circuit diagram of negative peak clipper is shown in figure.



**Case (i) :** consider for a diode  $R_f = 0$ ,  $R_r = \infty$ ,  $V_\gamma = 0$  (diode is an ideal one)

Now for the given circuit,  $V_D = V_i - (-V_R)$

If  $V_i > -V_R$ ,  $V_D = \text{positive value}$  so diode is in OFF state (replaced with open circuit)

Then  $V_O = V_i$

If  $V_i < -V_R$ ,  $V_D = \text{negative value}$  so diode is in ON state (replaced with short circuit)


Then  $V_O = -V_R$

Here the input waveform below the reference level ( $-V_R$ ) has been clipped means negative peak (positive base) of the input signal is clipped.

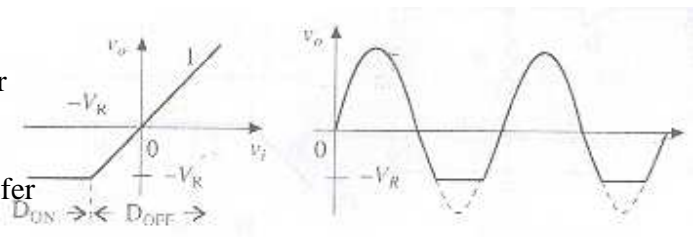**Transfer characteristics:**

If  $V_i > -V_R$ , Then  $V_O = V_i$  so slope of transfer characteristics curve is one

If  $V_i < -V_R$ , Then  $V_O = -V_R$  so slope of transfer characteristics curve is zero



**Case (ii) :** consider for a diode  $R_f = 0$ ,  $R_r = \infty$ ,  $V_\gamma \neq 0$  (by replacing diode with simplified equivalent circuit)

Now for the given circuit,  $V_D = V_i - [-(V_R + V_\gamma)]$

If  $V_i > -(V_R + V_\gamma)$ ,  $V_D = \text{positive value}$  so diode is in OFF state

Then  $V_O = V_i$

If  $V_i < -(V_R + V_\gamma)$ ,  $V_D = \text{negative value}$  so diode is in ON state

Then  $V_O = -(V_R + V_\gamma)$

Here the input waveform below the level  $-(V_R + V_\gamma)$  has been clipped

**Transfer characteristics:**

If  $V_i > -(V_R + V_\gamma)$ , Then  $V_O = V_i$  so slope of transfer characteristics curve is one

If  $V_i < -(V_R + V_\gamma)$ , Then  $V_O = -(V_R + V_\gamma)$  so slope of transfer characteristics curve is zero

**Case (iii) :** consider for a diode  $R_f \neq 0$ ,  $R_r = \infty$ ,  $V_\gamma \neq 0$  (by replacing diode with piece wise linear equivalent circuit)

Now for the given circuit,  $V_D = V_i - [-(V_R + V_\gamma)]$

If  $V_i > -(V_R + V_\gamma)$ ,  $V_D =$  positive value so diode is in OFF state  
Then  $V_O = V_i$

If  $V_i < -(V_R + V_\gamma)$ ,  $V_D =$  negative value so diode is in ON state

$$V_O = -(V_R + V_\gamma) + i R_f$$

$$V_O = -(V_R + V_\gamma) + (R_f / R + R_f) [V_i - (V_R + V_\gamma)]$$

$$V_O = -(V_R + V_\gamma)(R / R + R_f) + V_i (R_f / R + R_f)$$

$$V_O = -(V_R + V_\gamma) + V_i (R_f / R + R_f) \text{ by considering } R \text{ is large.}$$

Here the input waveform below the level  $-(V_R + V_\gamma)$  may not be clipped completely. means negative peak(positive base) of the input signal is not clipped totally.

### Transfer characteristics:

If  $V_i > -(V_R + V_\gamma)$ , Then  $V_O = V_i$  Then slope of transfer characteristics curve is one.

If  $V_i < -(V_R + V_\gamma)$ , then  $V_O = -(V_R + V_\gamma) + V_i (R_f / R + R_f)$  so slope of transfer characteristics curve is  $R_f / R + R_f$