

### Step voltage input to attenuator:

Consider source resistance is zero.

For  $t < 0$ ,  $V_i = 0$  V, so  $V_o = 0$  V

At  $t = 0^+$ ,  $V_i = V$  volts (there is a sudden change in input voltage)

here an infinite current will flows through the capacitors  $C_1$  and  $C_2$  so some voltage will be existed across  $C_1$  and  $C_2$ .

Assume  $V_1$  and  $V_2$  are voltage across capacitors  $C_1$  and  $C_2$

By applying KVL,  $V = V_1 + V_2$

$$V = q / C_1 + q / C_2$$

$$V_o(0^+) = V_2 = q / C_2 = VC_1 / (C_1 + C_2)$$

At  $t = \infty$  (for  $t > 0$ ), capacitors are replaced with open circuit

So final output voltage  $V_o(\infty) = V R_2 / (R_1 + R_2)$

We know for step input, voltage at  $t = 0^+$  and voltage at  $t = \infty$  is same, similarly for perfect compensation output voltage at  $t = 0^+$  and voltage at  $t = \infty$  is must be same


Then  $V_o(0^+) = V_o(\infty)$

$$VC_1 / (C_1 + C_2) = V R_2 / (R_1 + R_2)$$

$$R_1 C_1 = R_2 C_2$$

$$C_1 = R_2 C_2 / R_1 = C_P$$

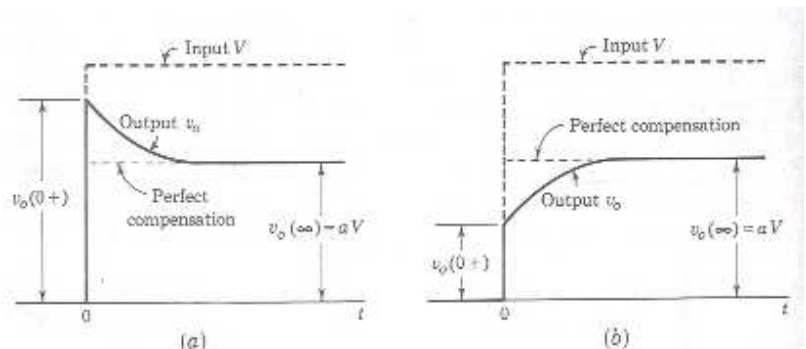Where  $C_P$  is the required value of  $C_1$  for perfect compensation.



If  $C_1 > C_P$ , the attenuator is said to be over compensated because initial output voltage is more compared to the final output voltage.

If  $C_1 < C_P$ , the attenuator is said to be under compensated because initial output voltage is small compared to the final output voltage.

Time taken by the over compensated or under compensated waveforms to reach its final value is  $2.2 RC$ , where  $R = R_1 R_2 / (R_1 + R_2)$  and  $C = C_1 + C_2$ .

### Problems on attenuators:

1. calculate and plot the output waveform for

K.Chiranjeevi, Asst. Prof, ECE Dept, GMRIT

(i)  $C = 100 \text{ PF}$       (ii)  $C = 150 \text{ PF}$       (i)  $C = 50 \text{ PF}$   
 Here input is 25V step.


We know For perfect compensation ,  $C_p = R_2 C_2 / R_1 = 100 \text{ PF}$

Case (i):  $C = 100 \text{ PF} = C_p$

It represents attenuator is under perfect compensation. so

$$V_o(0^+) = V C_1 / (C_1 + C_2) = V_o(\infty) = 12.5 \text{ V}$$

Case(ii):  $C = 150 \text{ PF} > C_p$

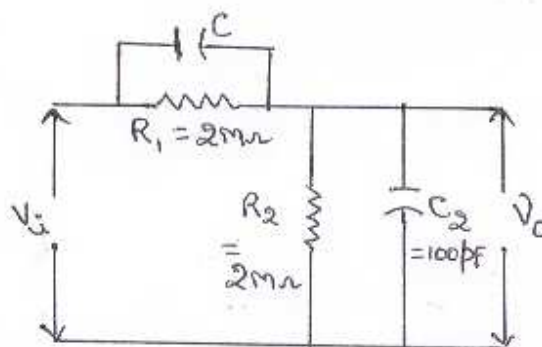

It represents attenuator is under over compensation


$$\text{So } V_o(0^+) = V C_1 / (C_1 + C_2) = 15 \text{ V}$$

$$\text{And } V_o(\infty) = V R_2 / (R_1 + R_2) = 12.5 \text{ V}$$

Time taken by the over compensated waveform to reach its

Final value = 550  $\mu\text{sec}$

Case(ii):  $C = 50 \text{ PF} < C_p$

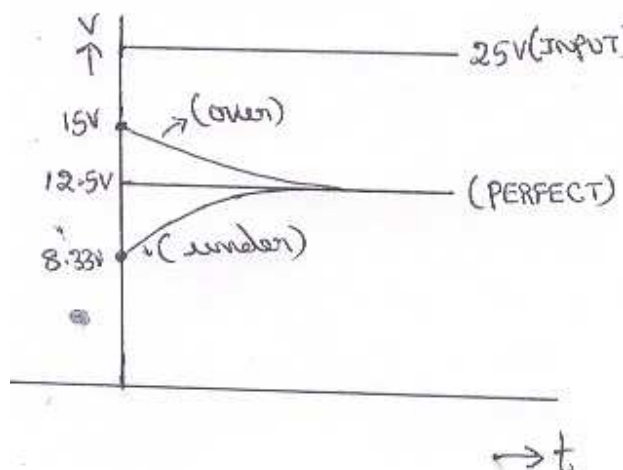

It represents attenuator is under compensated.

$$\text{So } V_o(0^+) = VC_1 / (C_1 + C_2) = 8.33 \text{ V}$$

$$\text{And } V_o(\infty) = V R_2 / (R_1 + R_2) = 12.5 \text{ V}$$

Time taken by the under compensated waveform to reach its

Final value = 330  $\mu$ sec