

**Statement:** The area under the output waveform above the axis is equal to the area below the axis for pulse input to high pass RC circuit.

**Proof:**

Area under the output above the axis ,  $A_1 = \int_0^{t_p} V_o(t) dt$

$$A_1 = \int_0^{t_p} V e^{-t/RC} dt$$

$$A_1 = VRC (1 - e^{-t_p/RC})$$

Area under the output below the axis ,  $A_2 = \int_{t_p}^{\infty} V_o(t) dt$


$$A_2 = \int_{t_p}^{\infty} V(e^{-t/RC} - 1) e^{-(t-t_p)/RC} dt$$

$$A_2 = -VRC (1 - e^{-t_p/RC})$$

So  $A_1 = A_2$

Hence proved.

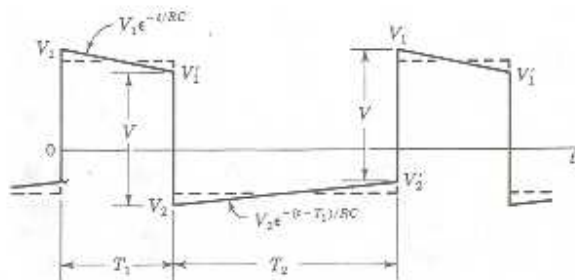**Square wave input:** steady state output waveform for square wave input is shown in figure.(operation of the circuit is same as pulse input)



**Expressions for steady state voltages:**

From the output waveform ,  $V_1' = V_1 e^{-T_1/RC}$

$$V_2' = V_2 e^{-T_2/RC}$$

$$V_1 - V_2' = V$$

$$V_1' - V_2 = V$$

**Statement:** for any periodic input waveform to high pass RC circuit, the average level of the steady state output waveform is always zero irrespective of the input average level.

**Proof:**

By applying KVL to the loop,

$$v_i(t) = \frac{1}{C} \int i dt + V_o(t) \text{ and } i = V_o(t)/R$$

$$d v_i(t)/dt = V_o(t)/RC + d V_o(t)/dt$$

integrating with respect to t between the limits 0 to T is


$$v_i(T) - v_i(0) = \int_0^T (V_o(t)/RC) dt + V_o(T) - V_o(0)$$

but we know for periodic waveform,  $v_i(T) = v_i(0)$

$$V_o(T) = V_o(0) \text{ so } \int_0^T (V_o(t)/RC) dt = 0$$

$$\int_0^T V_o(t) dt = 0$$

Hence proved.

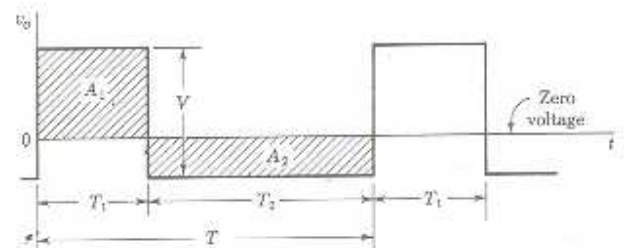


**Symmetrical square wave input :**

For symmetrical square wave input  $T_1 = T_2$  so  
 $V_1' = V_1 e^{-T/2RC}$

$$V_2' = V_2 e^{-T/2RC}$$

And also  $V_1 = -V_2$
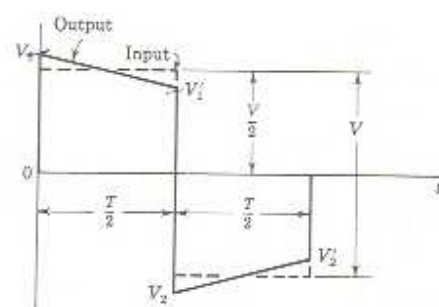
$$V_1' = -V_2' \text{ (since from the above statement)}$$



**Percentage tilt of the output waveform:**

Percentage tilt is defined by  $p = \{V_1 - V_1' / (V/2)\} \times 100$

We know  $V_1' - V_2 = V$

$$V_1' + V_1 = V$$

$$V_1 e^{-T/2RC} + V_1 = V$$

$$V_1 = V / 1 + e^{-T/2RC} \text{ -----(1)}$$

$$V_1' = V_1 e^{-T/2RC}$$

$$V_1' = e^{-T/2RC} V / 1 + e^{-T/2RC} \text{ -----(2)}$$

$$\text{So } p = [(1 - e^{-T/2RC}) / (1 + e^{-T/2RC})] \times 100$$

(by using equations 1 and 2)

$$\text{If } T/2RC \ll 1 \text{ then } p = [T/2RC] \times 100$$

$$p = [1/2fRC] \times 100$$

$$p = [\pi f_l / f] \times 100$$

where  $f_l$  is the lower cutoff frequency of high pass RC circuit.