 


**Diode OR gate for positive logic:**

A diode OR for positive logic is shown in figure below . This is same as diode OR gate

for negative logic except that all diodes must be reversed. Consider

The supply voltage  $V_R$  has a value equal to the voltage  $V(0)$  of the 0 state.  
(for positive logic  $V(0)$  is at low potential)



Initially equation for output voltage is  $v_o = V(0) + IR$  ----(1)

Since current direction is from anode to cathode.

**Case(i):** If all inputs (A ,B,...N) are in the 0 state, then the voltage across each diode is

$V(0) - V(0) = 0$  . Since in order for a diode to conduct it must be forward-biased by

Atleast the cut-in voltage  $V_\gamma$ , then none of the diode conducts. So current flowing

Through the circuit is zero.

Hence the output voltage is  $v_o = V(0)$  , and Y is in the 0 state.


**Case(ii):** If the inputs B,...N are in 0 state and , input A is changed to the 1 state, which

for positive logic is at the potential  $V(1)$ , more positive than the 0 state, then D1 will

conduct and remaining diodes are in non conducting state. Then the circuit diagram will

Becomes as shown below. ( by replacing D1 with its piece wise linear equivalent

 Circuit & And D2...DN with open circuit).



By applying KVL to the above loop,

$$I = \frac{V(1) - V_\gamma - V(0)}{R_s + R_f + R}$$

Then the output becomes,

$$v_o = V(0) + \left( \frac{V(1) - V_\gamma - V(0)}{R_s + R_f + R} \right) R$$

Usually  $R$  is chosen much larger than  $R_s + R_f$ . Under this restriction

$$v_o = V(1) - V_\gamma$$

Hence the output voltage is smaller than the most positive value of  $V(1)$  by  $V_\gamma$ .

If diode is an ideal one, then  $v_o = V(1)$

So OR function for positive logic is satisfied with the above circuit.

### AND Gate:

An AND gate has two or more inputs and a single output, and it operates in accordance with the following definition.

The output of an AND assumes the 1 state if and only if all the inputs assume the 1 state.

The IEEE standard symbol for the AND circuit is given in figure (a) Below together with the Boolean expression for the gate. The equation is to be read

“Y equals A and B and.....and N”. It may be verified that the two-input

Truth table of figure(b) is consistent with the above definition of the AND operation.

