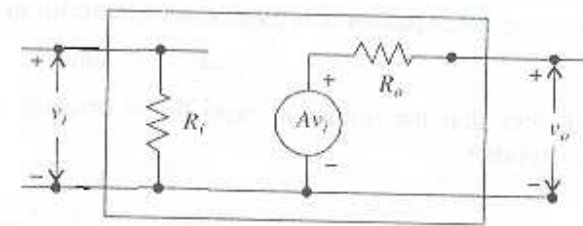


Expression for sweep error in Bootstrap sweep circuit:


We know
$$e_s = \frac{V_s}{V_o(t = \infty)} \text{-----(1)}$$

Equivalent circuit of voltage amplifier is,



In bootstrap sweep circuit , by replacing voltage amplifier with its equivalent circuit,

The resultant circuit is shown below

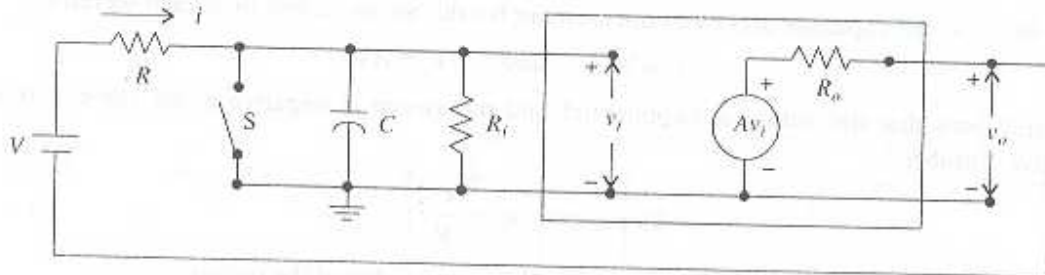


For an voltage amplifier , output resistance is low.

And at $t = \infty$ capacitor is replaced With an open circuit.

So by neglecting R_o and by replacing capacitor with an open circuit the above circuit is

redrawn as shown below

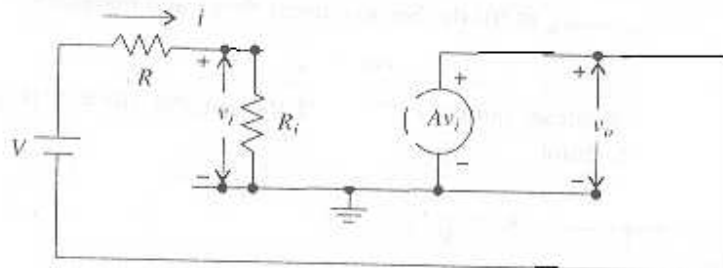

From the circuit (at $t = \infty$), $V_o = AV_i \text{-----(2)}$

Here $V_i = i R_i \text{-----(3)}$

By applying KVL,

$$V - iR - iR_i + V_o = 0$$

$$i = \frac{V + V_o}{R + R_i} \text{-----(4)}$$

From equations (2) (3) &(4),

$$V_o = A \left(\frac{V + V_o}{R + R_i} \right) R_i$$

$$V_o = \frac{AV R_i}{R + R_i(1 - A)} \text{-----(5)}$$

From equations (1) &(5) ,

$$e_s = \frac{V_s (R + R_i(1 - A))}{AR_i V}$$

$$e_s = \frac{V_s}{AV} \left(\frac{R}{R_i} + (1 - A) \right)$$

If $A = 1$, then


$$e_s = \frac{V_s}{V} \left(\frac{R}{R_i} \right)$$

Here sweep error is minimum when only input impedance of an amplifier is high.

Sweep error in Miller sweep circuit:

In miller sweep circuit , by replacing voltage amplifier with its equivalent circuit,


The resultant circuit is shown below

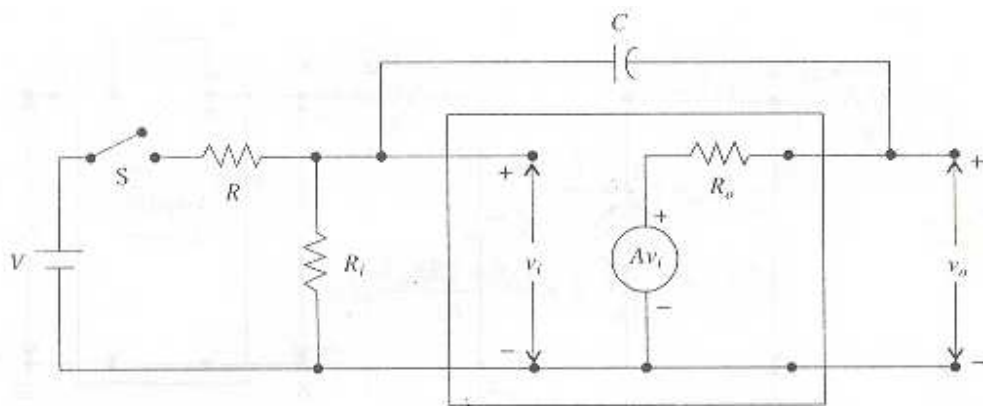

For an voltage amplifier , output resistance is low.

And at $t = \infty$ capacitor is replaced With an open circuit.

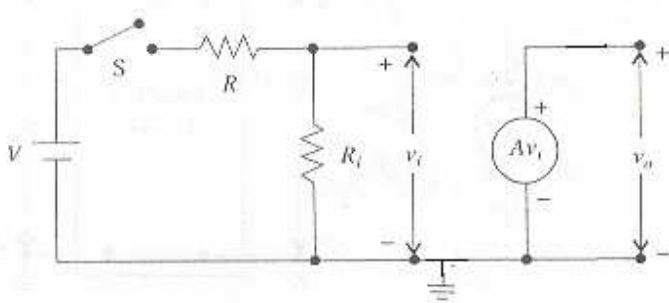So by neglecting R_O and by replacing capacitor with an open circuit the above circuit is redrawn as shown below



From the circuit (at $t = \infty$), $V_o = AV_i$

Here
$$V_i = \frac{VR_i}{R + R_i}$$

So output voltage at $t = \infty$ is
$$V_o = \frac{AVR_i}{R + R_i}$$

Therefore sweep error ,

$$e_s = \frac{V_s(R + R_i)}{AR_iV}$$

$$e_s = \frac{V_s}{AV} \left(\frac{R}{R_i} + 1 \right)$$

Here gain must be high. So sweep error is low.

In miller sweep circuit , to reduce sweep error input impedance of an amplifier need not be high.