

Different linear networks are

1. RC circuits
2. RL circuits
3. RLC circuits


RC circuits: 1.High pass RC circuit

1. Low pass RC circuit

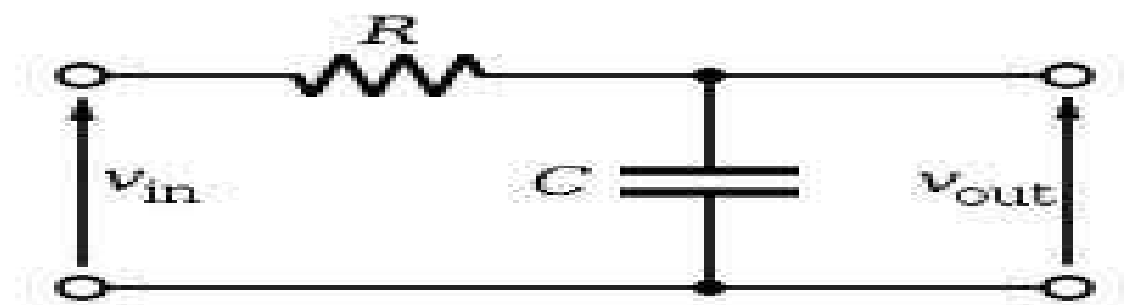1.High pass RC circuit: in an RC circuit if capacitor is in series with the input voltage signal and a resistor is in shunt with the output then that circuit is named as high pass RC circuit.

Operation : we know $X_c = 1/2\pi f C$

If frequency of input signal is low ,capacitive reactance is high ,then Capacitor is replaced with an open circuit .so output voltage is zero.



Similarly If frequency of input signal is high ,capacitive reactance is low ,then Capacitor is replaced with an short circuit .so output voltage is same as input voltage.

Hence it behaves like a high pass RC circuit.

Sinusoidal input: the sinusoidal input is defined as $v_i(t) = V_m \sin \omega t$

Applying KVL around the loop

$$v_i(t) - \frac{1}{C} \int i \, dt - i R = 0$$

$$V_i(s) = I(s) [R + 1/sC]$$

$$V_o(s) = I(s) R$$

$$V_o(s)/V_i(s) = 1/(1 + 1/sRC) = 1/(1 - j(1/2\pi f R C))$$


So gain of a circuit is $A = 1/\sqrt{1+(f_1/f)^2}$

Where $f_1 = 1/2\pi RC$ = lower cutoff frequency

Phase angle = $\tan^{-1}(f_1/f)$

So for an high pass RC circuit if input is a sinusoidal then output is also sinusoidal.

Frequency response:

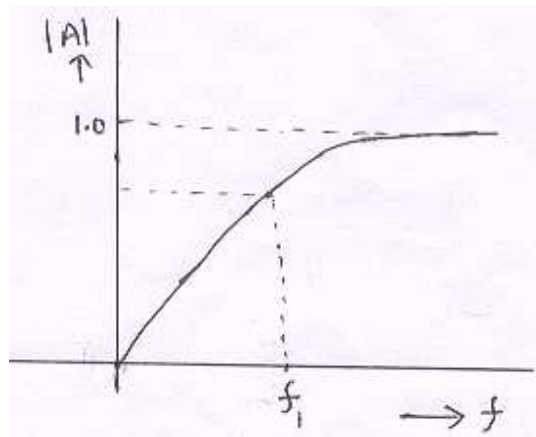

Note :

1. voltage across the capacitor does not changes instantaneously
2. capacitor takes some finite amount of time for its charging or discharging
3. The time required for the charging or discharging of a capacitor can be specified by a time constant of a circuit.
4. time constant is the product of total resistance and capacitance associated in the given circuit.

Step voltage input :

For an high pass RC circuit we know $V_o = V_i - V_c$,

Where V_c is the voltage across the capacitor.


Case(i): for step voltage input we know for $t < 0$, $V_i = 0 \text{ V}$, $V_c = 0 \text{ V}$ so $V_o = 0 \text{ V}$

Case(ii): at $t = 0^-$ (immediately before $t = 0$) still output voltage is zero
but at $t = 0^+$ (immediately after $t = 0$) , $V_i = V \text{ Volts}$, $V_c = 0 \text{ V}$ so $V_o = V \text{ Volts}$

case(iii): for $t > 0$, voltage across the capacitor increases exponentially (by doing mathematical analysis we can get current is in the form of exponential) so output is a decaying exponential.

Time constant of an high pass RC circuit is RC (by neglecting source resistance).
 If time constant is high then output takes more time to reach final value similarly
 If time constant is low then output takes less time to reach final value.

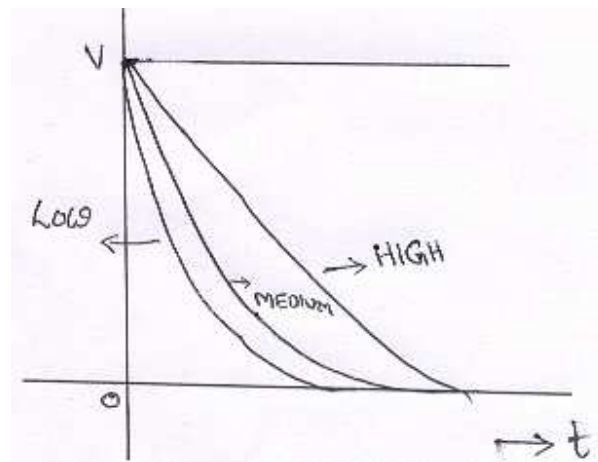Output waveforms for different time constants is shown below



Pulse input to high pass RC circuit :

Case(i): for $t < 0$ and also at $t = 0^-$, $V_i = 0$ V, $V_c = 0$ V so $V_o = 0$ V

Case(ii): at $t = 0^+$ (immediately after $t = 0$), $V_i = V$ Volts, $V_c = 0$ V so $V_o = V$ Volts

case(iii): during the interval 0 to t_p , voltage across the capacitor increases exponentially (by doing mathematical analysis we can get current is in the form of exponential) so output is a decaying exponential.

Equation for output voltage during 0 to t_p is $V_o(t) = V e^{-t/RC}$

At $t = t_p$, $V_o(t) = V e^{-t_p/RC} = V_p$

Case(iv): at $t = t_p^+$, input voltage reduces by an amount of V volts so output will also

Reduces by the same amount (because V_c can not changes instantaneously).

So at $t = t_p^+$, $V_o(t) = V_p - V$ (it is a negative magnitude)


Case(v): for $t > t_p$, $V_i = 0$ V so capacitor will discharges then output will tries to approach zero volts.

We know equation for exponential signal is $V_o(t) = V_f + (V_i - V_f) e^{-(t-t_x)/\tau}$


For $t > t_p$, $V_f = 0$ V, $t_x = t_p$, $V_i = V_p - V$ then $V_o(t) = (V_p - V) e^{-(t-t_p)/RC}$

$$V_o(t) = V(e^{-t_p/RC} - 1) e^{-(t-t_p)/RC}$$

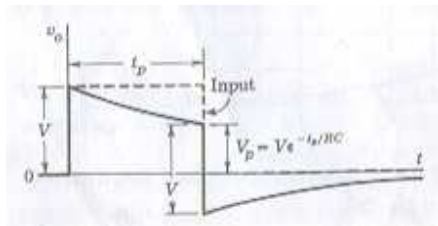
The waveforms for different time constants as shown below,
(Medium)



(high)

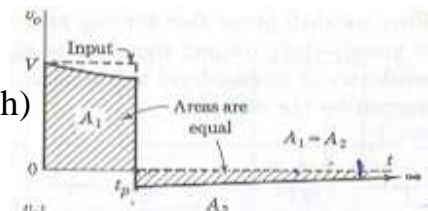

(low)

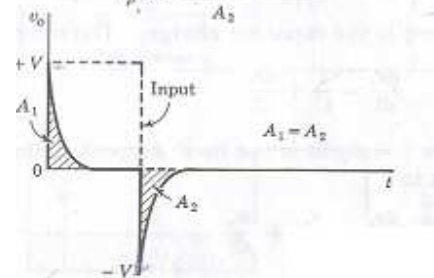

The process of converting pulses into spikes by means of a circuit having short time constant is known as a peaking.