


Design of Monostable Multivibrator:

Circuit diagram is shown below.


This circuit is not symmetrical . so here we need to consider both states of the device.

We know initial state of the device is

Q1 OFF & Q2 ON (Stable state)

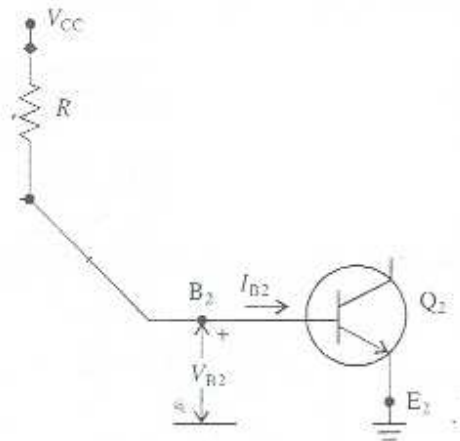

Collector circuit of Q2

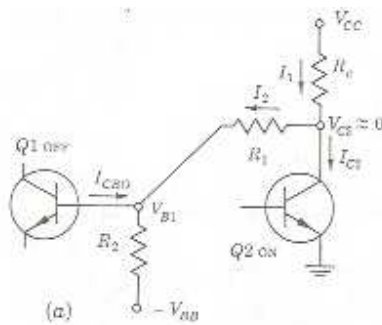

Base circuit of Q2

Since For DC analysis capacitors are replaced with an open circuit.

To keep Q1 is in OFF state , $V_{BE1} < V_{BE(cutoff)}$

From the collector circuit of Q2 , $V_{BE1} = V_{BE1}$ due to $V_{CE(sat)} + V_{BE}$ due to $-V_{BB}$

$$V_{BE1} \text{ due to } V_{CE(sat)} = \frac{V_{CE(sat)} R_2}{R_1 + R_2}$$

$$V_{BE1} \text{ due to } -V_{BB} = \frac{-V_{BB} R_1}{R_1 + R_2}$$

$$V_{BE1} = \frac{-V_{BB}R_1}{R_1 + R_2} + \frac{V_{CE(sat)}R_2}{R_1 + R_2}$$

So
$$\frac{-V_{BB}R_1}{R_1 + R_2} + \frac{V_{CE(sat)}R_2}{R_1 + R_2} < V_{BE(cutoff)} \text{ ----- (1)}$$

To keep Q2 is in ON state, $I_{B2} \geq I_{B2(min)}$

Where
$$I_{B2(min)} = \frac{I_{C2}}{h_{FE}}$$

From the collector circuit of Q2 , $I_{C2} = I_1 - I_2$

$$I_{C2} = \left(\frac{V_{CC} - V_{CE(sat)}}{R_C} \right) - \left(\frac{V_{CE(sat)} - (-V_{BB})}{R_1 + R_2} \right)$$

$$I_{B2(min)} = \frac{1}{h_{FE}} \left(\left(\frac{V_{CC} - V_{CE(sat)}}{R_C} \right) - \left(\frac{V_{CE(sat)} - (-V_{BB})}{R_1 + R_2} \right) \right) \text{ ----- (2)}$$

From the base circuit of Q2 ,


$$I_{B2} = \left(\frac{V_{CC} - V_{BE(sat)}}{R} \right)$$

Therefore, we know the necessary condition to keep the transistor in ON state is


$$\left(\frac{V_{CC} - V_{BE(sat)}}{R} \right) \geq \frac{1}{h_{FE}} \left(\left(\frac{V_{CC} - V_{CE(sat)}}{R_C} \right) - \left(\frac{V_{CE(sat)} - (-V_{BB})}{R_1 + R_2} \right) \right) \text{ -- (3)}$$

Other state of the monostable multivibrator is Q1 ON & Q2 OFF (Quasi stable state)

Collector circuit of Q1

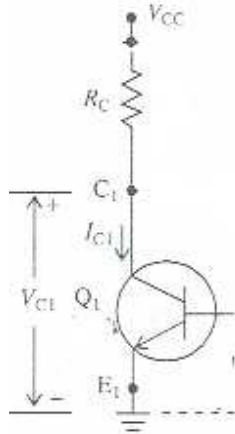

Base circuit of Q1 is

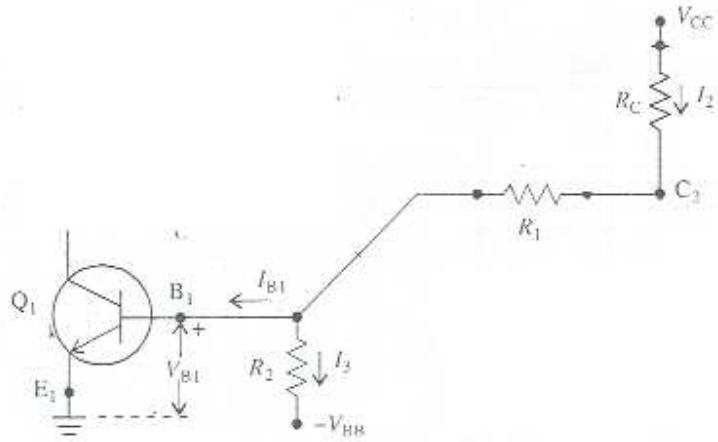

To keep Q1 is in ON state, $I_{B1} \geq I_{B1(\min)}$

Where
$$I_{B1(\min)} = \frac{I_{C1}}{h_{FE}}$$

From the collector circuit of Q1 ,

$$I_{C1} = \left(\frac{V_{CC} - V_{CE(sat)}}{R_C} \right)$$

$$I_{B1(\min)} = \frac{1}{h_{FE}} \left(\frac{V_{CC} - V_{CE(sat)}}{R_C} \right)$$

From the base circuit of Q1 , $I_{B1} = I_2 - I_3$

$$I_{B1} = \left(\frac{V_{CC} - V_{BE(sat)}}{R_C + R_1} \right) - \left(\frac{V_{BE(sat)} - (-V_{BB})}{R_2} \right)$$

Therefore, we know the necessary condition to keep the transistor in ON state is

$$\left(\frac{V_{CC} - V_{BE(sat)}}{R_C + R_1} \right) - \left(\frac{V_{BE(sat)} - (-V_{BB})}{R_2} \right) \geq \frac{V_{CC} - V_{CE(sat)}}{R_C h_{FE}} \quad \text{----(4)}$$

Here there is no need to check the status of Q2 since voltage at base terminal of Q2 varies

From time to time(this is not a fixed value).

MONO STABLE

UNIT-5

Capacitor value should be selected from $T = 0.693 RC$ -----(5)

Component values should be selected to satisfy equations (1),(2),(4) & (5)