

### Ramp input:

We know for an high pass RC circuit,  


$$d v_i(t)/dt = V_o(t)/RC + d V_o(t)/dt$$
 but here  $v_i(t) = \alpha t$

$\alpha = V_o(t)/RC + d V_o(t)/dt$  it is a first order differential equation  
 by solving this equation ,

$$V_o(t) = \alpha RC (1 - e^{-t/RC})$$

If  $RC \ll T_s$  , then  $V_o(t) = \alpha RC$

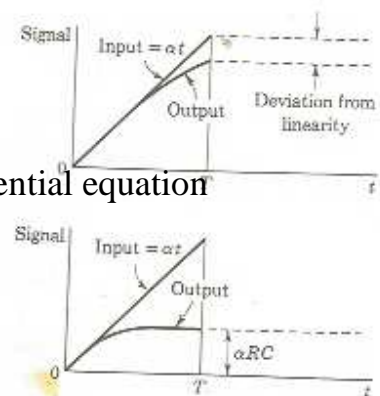If  $RC \gg T_s$  , then  $V_o(t) = \alpha t [1 - (t/2RC)]$



### High pass RC circuit as a differentiator:

For high pass RC circuit,

$$v_i(t) = \frac{1}{c} \int i dt + V_o(t)$$

if RC is low then voltage across the capacitor is maximum and output voltage is almost zero . so  $v_i(t) = \frac{1}{c} \int i dt$

$$\text{So } i = c d v_i(t)/dt$$

$$V_o(t) = RC d v_i(t)/dt \text{ since } V_o(t) = iR$$

Hence high pass RC acts as a differentiator when  $RC \ll T$

It produces spikes by taking square wave input.

### Problems on high pass RC circuit:

1. the pulse from a high voltage generator raises linearly for  $0.01 \mu\text{sec}$  and then remains constant for  $2 \mu\text{sec}$ . The rate of rise of the pulse is measured with an RC differentiating circuit whose time constant is 200 pico secs. if the positive output voltage from the differentiator as a maximum value of 60 V .determine peak value of the generator.

#### Solution:


From the given data input waveform to high pass is ramp signal

$$\text{So } V_o(t) = \alpha RC (1 - e^{-t/RC}) \text{ but here } RC \ll T_s$$

$$\text{So } V_o(t) = \alpha RC$$

$$\text{Then } \alpha = V_o(\text{max})/RC = 3 \times 10^{11}$$
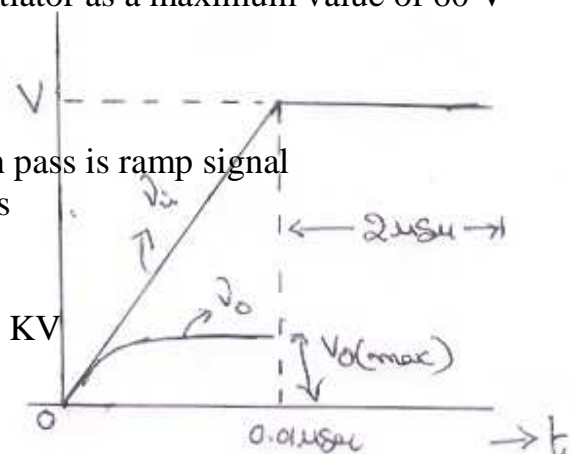
$$\text{Hence peak value of the generator } V_i = \alpha T_s = 3 \text{ KV}$$



2. A limited ramp of  $V$  volts is applied to an RC differentiator circuit .what is the peak value of the output waveform for (a)  $T = RC$  (b)  $T = 0.2 RC$  (c)  $T = 5 RC$  .

**Solution;**


Here  $V_o(t) = \alpha RC (1 - e^{-t/RC})$  and  $\alpha = V/T$

Peak value of output is  $V_o(T) = VRC (1 - e^{-T/RC})/T$

(a) if  $T = RC$  then  $V_o(T) = 0.632V$  volts

(b) if  $T = 0.2RC$  then  $V_o(T) = 0.9063V$  volts

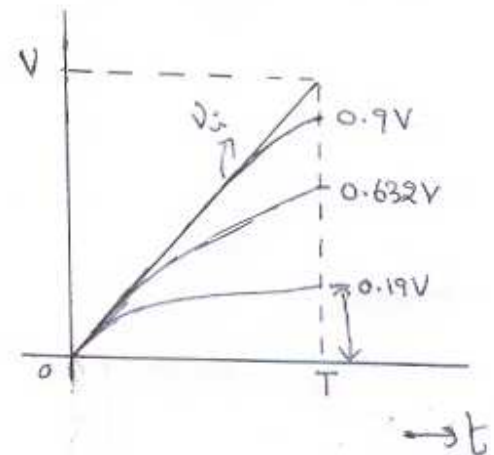(c) if  $T = 5RC$  then  $V_o(T) = 0.1986V$  volts



2. a 10 Hz symmetrical square wave is applied to an RC circuit .calculate and plot the output waveform under the following conditions. The lower 3-dB frequency is

(a) 0.3 Hz (b) 3 Hz (c) 30 Hz

**Solution:**

For symmetrical square wave input to high pass RC ,

$$V_1 = -V_2$$

$$V_1' = -V_2'$$

$$V_1' = V_1 e^{-T/2RC}$$

$$V_1 = V / (1 + e^{-T/2RC})$$

From the given data  $T = 0.1 \text{ sec}$


We know

$$f_1 = 1/2\pi RC \text{ so } RC = 1/2\pi f_1$$

$$(a) f_1 = 0.3 \text{ Hz then } RC = 0.5305 \text{ sec}$$

$$\text{so } V_1 = V / (1 + e^{-T/2RC}) = 0.523 \text{ V volts}$$
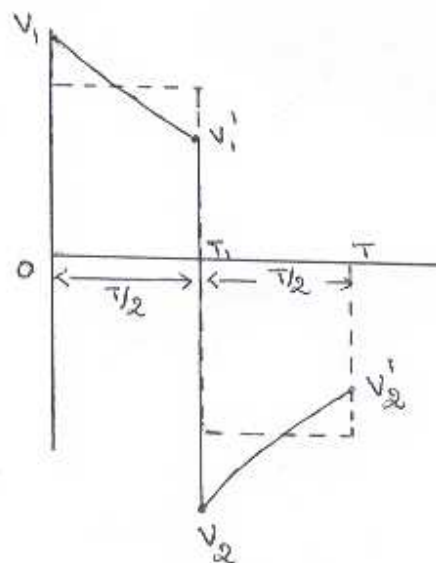
$$\text{and } V_1' = 0.476 \text{ V volts}$$



(b)  $f_1 = 3\text{Hz}$  then  $RC = 0.05305 \text{ sec}$   
 so  $V_1 = V / (1 + e^{-T/2RC}) = 0.7197 \text{ V volts}$   
 and  $V_1' = 0.328 \text{ V volts}$

(c)  $f_1 = 30\text{Hz}$  then  $RC = 5.305\text{m sec}$   
 so  $V_1 = V / (1 + e^{-T/2RC}) = 0.99 \text{ V volts}$   
 and  $V_1' = 0.432 \text{ V volts}$