

Problem:

The circuit given figure has the following parameters:

$V_{CC} = 20V, V_{EE} = 10V, R_e = 10K, R = 5K$ and $T_g = 700\mu\text{sec}$. the transistor h-parameter values are


$h_{ie} = 1.1K, h_{fe} = 50, \frac{1}{h_{oe}} = 40K$. a 20V sweep in 500 μsec is desired.

- (a) find a reasonable value for R_b (b) calculate C
(c) calculate return time (d) calculate sweep error
(e) calculate the recovery time T_1 for C_1 to recharge completely.

Solution:

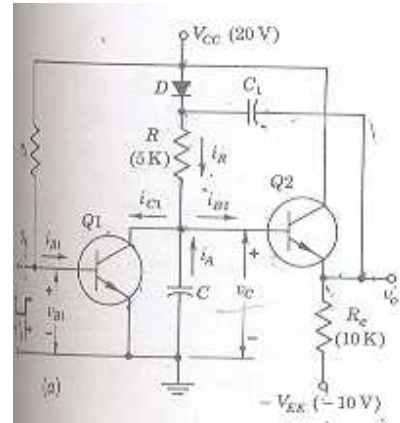(a) from equation(1), $R_b \leq h_{FE} R = 250 K$

hence, a reasonable value for R_b is 100 K



(b) since $T_s = 500 < T_g = 700\mu\text{sec}$, then equation (3) is valid,

$$\text{and } C = \frac{T_s}{R} = \frac{500}{5000} = 0.1\mu F$$

(c) from equation (4),

$$T_r = \frac{CV_s}{V_{CC} \left[\frac{h_{FE}}{R_b} - \frac{1}{R} \right]} = 333\mu\text{sec}$$

(d) we know for bootstrap sweep circuit,

$$e_s = \frac{V_s}{AV_{CC}} \left(\frac{R}{R_i} + (1 - A) \right)$$

$$\text{Here } A = 1 - \frac{h_{ie}}{R_i} \quad R_i = h_{ie} + A_I R_L$$

$$\text{And } A_I = \frac{1 + h_{FE}}{1 + h_{oe} R_L}$$

$$\text{Here } R_L = R_e$$

By substituting all the values , $A_f = 40.8, R_i = 409K, A = 0.9973$

And $e_s = 0.0149$

(e) from equation(5) , $T_1 = \frac{V_{CC}}{V_{EE}} \frac{R_e}{R} T$

$$T_1 = \frac{20}{10} \frac{10}{5} (700 + 333) = 4,130 \mu \text{sec}$$

Current Time-Base Generators:

We have mentioned earlier that Current time base generator is one that provides an Out put current waveform a portion of which exhibits a linear variation of current with time.

A linearly varying current waveform can be generated by applying a constant a constant Voltage across an inductor.(if inductor is an ideal one)

We know voltage across an inductor is $V = L \frac{di(t)}{dt}$

So
$$i(t) = \frac{1}{L} \int V dt$$

If V is constant then $i(t) = \frac{V}{L} t = \alpha t$

Hence $i(t)$ varies linearly with time.

But practically every inductor offers some resistance . so there is a need to apply


trapezoidal voltage across it to produce current sweeps.

Consider R_L is the resistance offered by the inductor L .

Then voltage across practical inductor is

$$V = R_L i(t) + L \frac{di(t)}{dt}$$

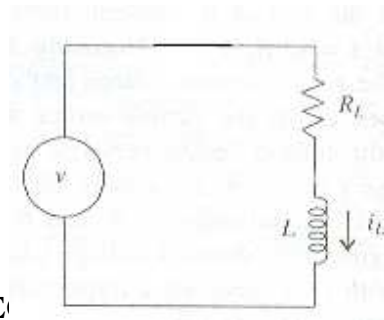If $i(t) = \alpha t$ then $V = R_L \alpha + L \alpha$



So $V = A + Bt$

Where $A = L\alpha$ and $B = \alpha R_L$

Hence trapezoidal voltage is essential to produce current sweeps across an practical inductor.