

Waveforms of the Astable Multivibrator:

We shall now explain the waveforms at both collector and bases.

Consider at $t=0$, Q1 OFF & Q2 ON ,

Assume that astable remains in this state for a time T_1 .

At $t = T_1$, the state of the device is Q1 ON & Q2 OFF

Also consider astable remains in this state for a time T_2 .

So the time period of astable is $T = T_1 + T_2$

Case(i):

At $t=0+$, Q1 OFF & Q2 ON ,

Here $v_{C2} = V_{CE(sat)}$


And $v_{B1} = V_{BE(sat)} - (V_{CC} - V_{CE(sat)})$

Due to the base spreading resistance of a transistor , a spike of amplitude δ appears at

Base terminal of Q2 and at collector terminal of Q1. (refer monostable multi)

After certain time (small) , $v_{C1} = V_{CC}$, $v_{B2} = V_{BE(sat)}$

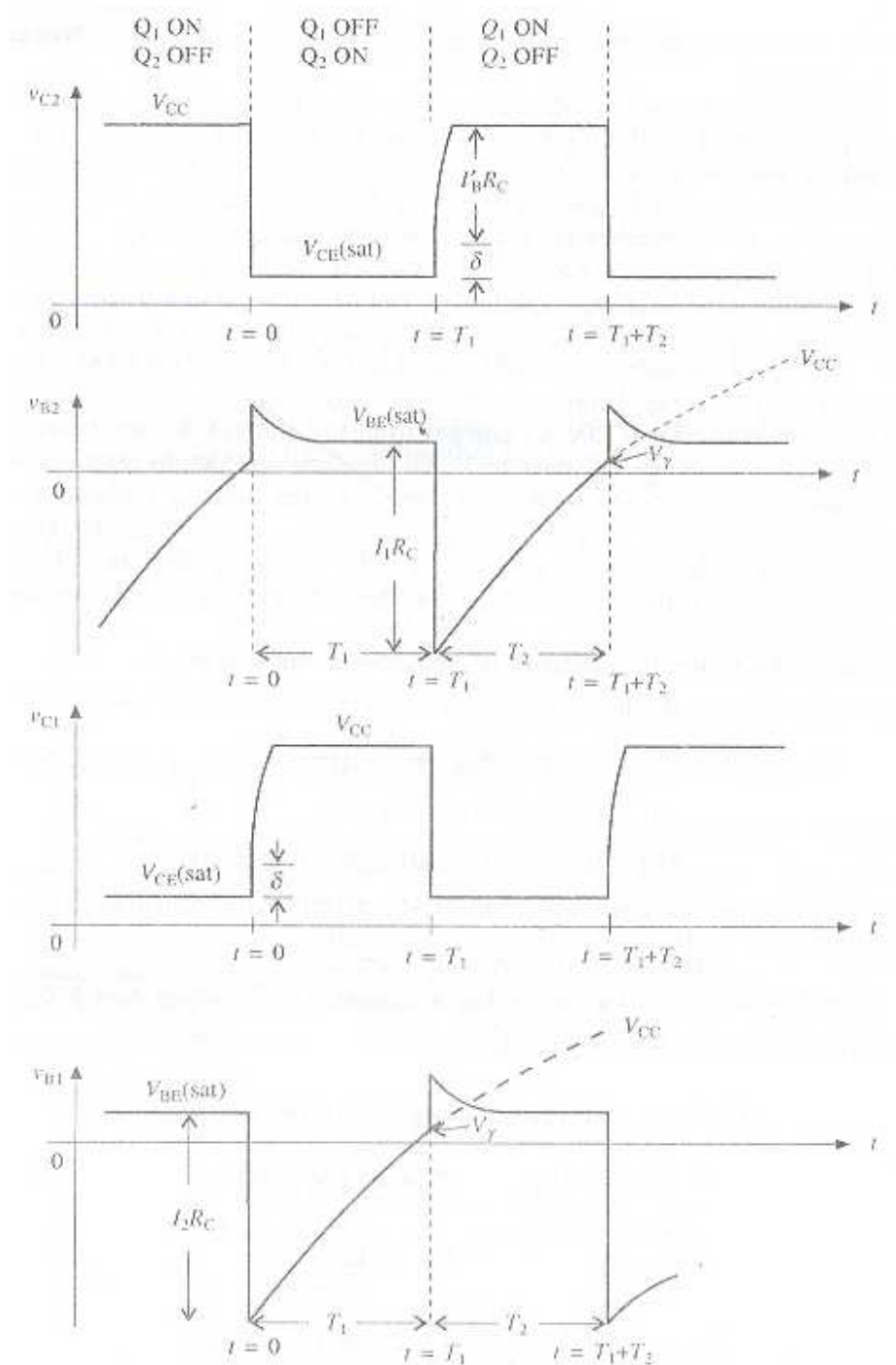During the interval 0 to T_1 , voltage at base terminal of Q1 increases exponentially with a time constant $R_1 C_1$ (by neglecting R_O). remaining voltage levels are constant



Case(ii):

At $t = T_1 +$, Q1 ON & Q2 OFF,

Here $v_{C1} = V_{CE(sat)}$

And $v_{B2} = V_{BE(sat)} - (V_{CC} - V_{CE(sat)})$

Due to the base spreading resistance of a transistor , a spike of amplitude δ appears at

Base terminal of Q1 and at collector terminal of Q2. (refer monostable multi)

After certain time (small) , $v_{C2} = V_{CC}, v_{B1} = V_{BE(sat)}$

During the interval T_1 to T_2 , voltage at base terminal of Q2 increases exponentially with a time constant R_2C_2 (by neglecting R_O). remaining voltage levels are constant.

Time period of an astable multivibrator:

From the above waveforms we know $T = T_1 + T_2$

We know time taken by the multivibrator to remain in one quasi stable state is $T = 0.693RC$ (from monostable multi)

So here $T_2 = 0.693R_2C_2$

And $T_1 = 0.693R_1C_1$

Hence $T = 0.693(R_2C_2 + R_1C_1)$

If $R_1 = R_2 = R$ and $C_1 = C_2 = C$ then $T = 1.386RC$