


PROBLEMS:

1. Calculate the stable-state currents and voltages for the circuit given below. Assume that the transistors have a minimum value of 20.


**Solution:**

Assume that Q1 is OFF & Q2 is ON

Base circuit of Q2 is

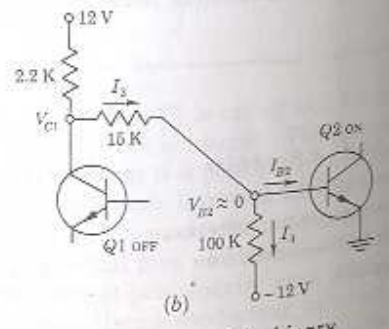

Collector circuit of Q2 is

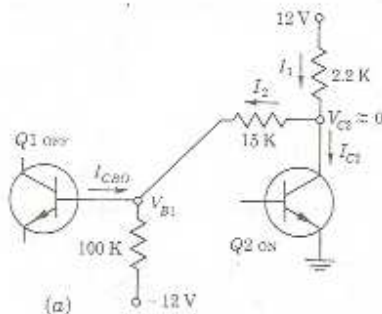


Assume that  $V_{CE(sat)} = V_{BE(sat)} = 0V$

From the above equations ,

$$V_{B1} = -1.56 V, \quad V_{B2} \approx 0V, \quad V_{C2} \approx 0V, \quad V_{C1} \approx 10.5V$$

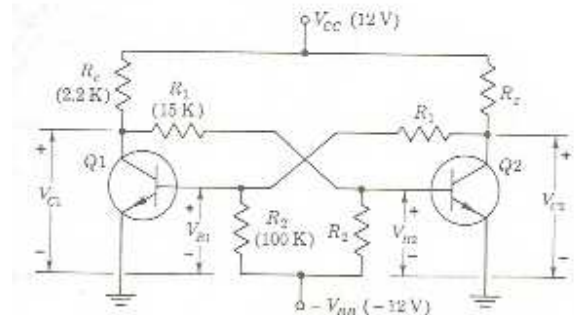
$$I_{C1} = 0mA, \quad I_{B1} = 0mA, \quad I_{C2} = 5.35mA, \quad I_{B2} = 0.58mA$$


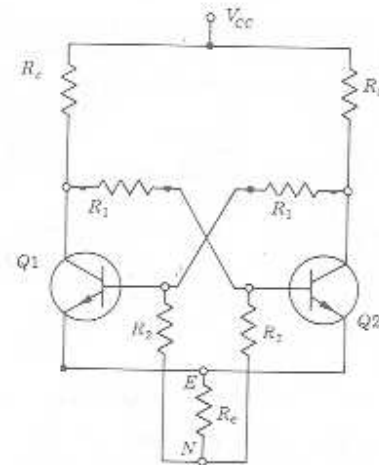
### Self bias binary :

The need for the negative power supply in fixed bias binary may be eliminated by using a common emitter resistor  $R_e$  to provide self bias , as shown in figure.

Operation of self bias binary is same as the operation of fixed bias binary.





### Design of self bias binary:

Consider stable state of binary is Q1 OFF & Q2 ON

Base circuit of Q2

Collector circuit of Q2

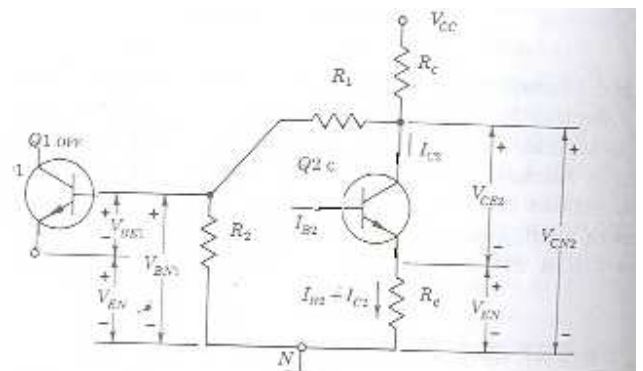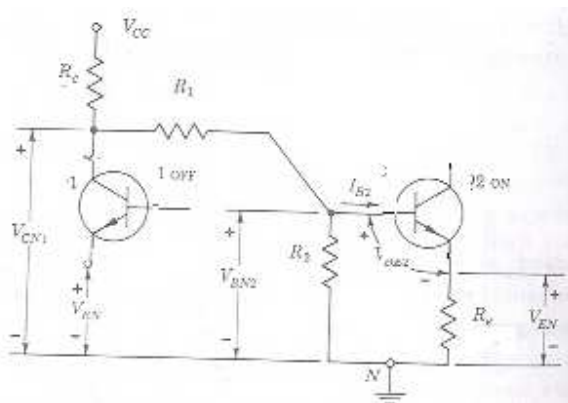

By determining Thevinan equivalent circuit at collector and base terminals of Q2 , Then the equivalent circuit when Q2 is in saturation is shown in figure below,

$$\text{Here } V_{Th} = \frac{V_{CC} R_2}{R_C + R_1 + R_2}$$

$$R_{Th} = \frac{R_2 (R_C + R_1)}{R_C + R_1 + R_2}$$

And also  $V_{Th} = \frac{V_{CC}(R_2 + R_1)}{R_C + R_1 + R_2}$


$$R_{Th} = \frac{R_C(R_2 + R_1)}{R_C + R_1 + R_2}$$

Now by applying KVL to the above loops, determine  $I_{B2}$ ,  $I_{C2}$ ,  $I_{E2}$  and

Also  $V_{EN} (= R_e I_{E2})$

We know To keep Q1 is in OFF state ,

$$V_{BE1} < V_{BE(cutoff)}$$

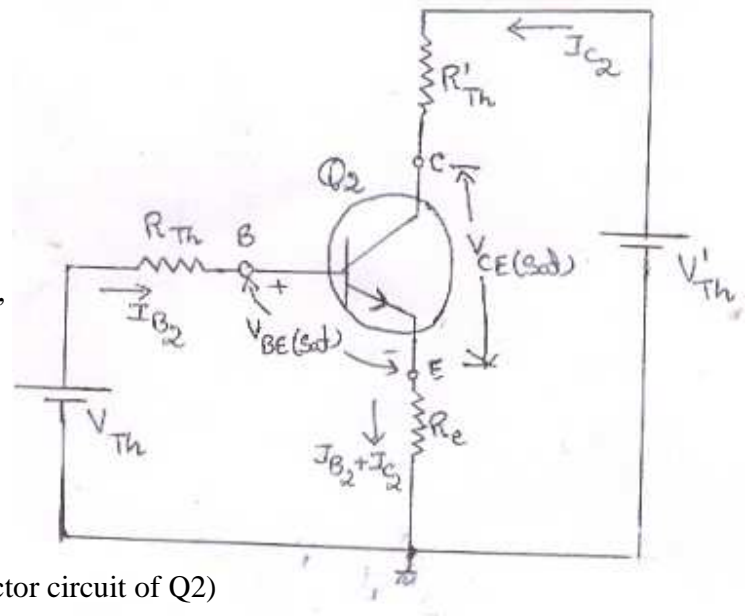

Here  $V_{BE1} = V_{BN1} - V_{EN}$  (from collector circuit of Q2)

Where  $V_{BN1} = \frac{V_{CN2}R_2}{R_1 + R_2}$  ,  $V_{CN2} = V_{CE(sat)} + V_{EN}$

To keep Q2 is in ON state ,  $I_{B2} \geq I_{B2(min)}$

Expression for  $I_{B2}$  &  $I_{C2}$  can be obtained from the above analysis.

And here  $I_{B2(min)} = \frac{I_{C2}}{h_{FE}}$

Hence the component values should be properly selected to satisfy the above two conditions.

### Expressions for steady state voltages and currents :

Assume that  $V_{CN1}$ ,  $V_{BN1}$  are voltages at collector and base terminals of Q1 respectively.

And  $V_{CN2}$ ,  $V_{BN2}$  are voltages at collector and base terminals of Q2 respectively.

$V_{EN}$  is the voltage at emitter terminals of both the transistors.

And also  $I_{C1}$  ,  $I_{C2}$ ,  $I_{B1}$  ,  $I_{B2}$ ,  $I_{E1}$ ,  $I_{E2}$  are the collector, base and emitter currents of corresponding transistors.

Consider stable state of self bias binary is **Q1 OFF & Q2 ON**

From the above analysis,

$$V_{CN2} = V_{CE(sat)} + V_{EN}$$

$$V_{BN2} = V_{BE(sat)} + V_{EN}$$

$$V_{BN1} = \frac{V_{CN2}R_2}{R_1 + R_2}$$

From the base circuit of Q2 ,

By using super position principle ,

$$V_{CN1} = V_{CN1} \text{ due to } V_{CC} + V_{CN1} \text{ due to } V_{BN2}$$

$$V_{CN1} \text{ due to } V_{BN2} = \frac{V_{BN2}R_C}{R_1 + R_C}$$

$$V_{CN1} \text{ due to } V_{CC} = \frac{V_{CC}R_1}{R_1 + R_C}$$

$$V_{CN1} = \frac{V_{BN2}R_C}{R_1 + R_C} + \frac{V_{CC}R_1}{R_1 + R_C}$$

And also the currents are ,

$$I_{C1} = 0mA, \quad I_{B1} = 0mA \quad I_{E1} = 0mA$$

$I_{C2}, I_{B2}, I_{E2}$  can be obtained by applying KVL to the equivalent circuit of Q2 when it is in saturation region .