

**Series clippers:** these are of two types

1. Clipping above the reference level
2. Clipping below the reference level

**Clipping above the reference level:**

Circuit diagram is shown below,

Consider diode is an ideal one.


Here  $V_D = V_i - V_R$

If  $V_i > V_R$ ,  $V_D = \text{positive value}$  so diode is in OFF state,

Then  $V_O = V_R$

If  $V_i < V_R$ ,  $V_D = \text{negative value}$  so diode is in ON state, Then  $V_O = V_i$

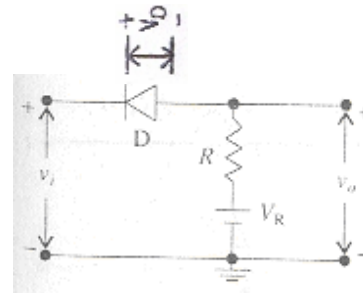Here the input waveform above the reference level ( $V_R$ ) has been clipped means positive peak(negative base )of the input signal is clipped.



**Transfer characteristics:**

It is a plot of output voltage as a function of input voltage.

If  $V_i > V_R$ , Then  $V_O = V_R$  so slope of transfer characteristics curve is zero(since output is independent of input).

If  $V_i < V_R$ , Then  $V_O = V_i$  so slope of transfer characteristics curve is one.

**Clipping below the reference level:**

Circuit diagram is shown below,

Consider diode is an ideal one.


Here  $V_D = V_i - V_R$

If  $V_i > V_R$ ,  $V_D = \text{positive value}$  so diode is in ON state,

Then  $V_O = V_i$

If  $V_i < V_R$ ,  $V_D = \text{negative value}$  so diode is in ON state, Then  $V_O = V_R$

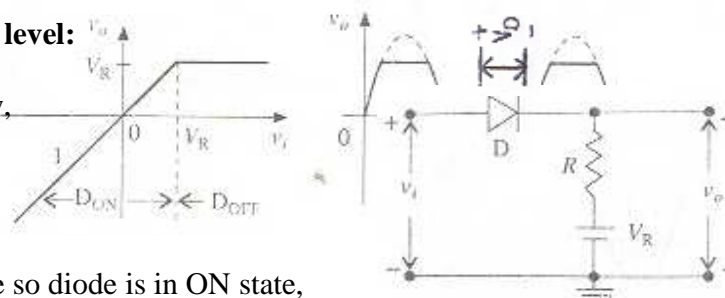Here the input waveform below the reference level ( $V_R$ ) has been clipped means negative peak(negative base )of the input signal is clipped.




**Transfer characteristics:**

It is a plot of output voltage as a function of input voltage.

If  $V_i > V_R$ , Then  $V_O = V_i$  so slope of transfer characteristics curve is one

If  $V_i < V_R$ , Then  $V_O = V_R$  so slope of transfer characteristics curve is zero.

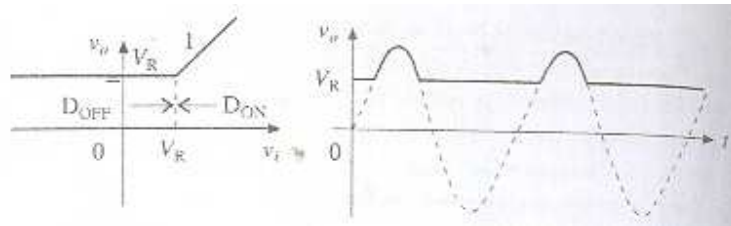
**Clipping at two independent levels (two level slicer) :**

Circuit diagram is shown below,

Assume diodes are ideal.

Here  $V_{D1} = V_i - V_{R1}$

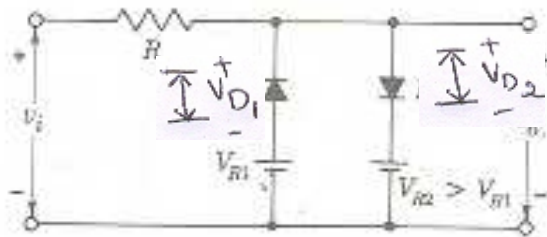And  $V_{D2} = V_i - V_{R2}$   
(assume  $V_{R2} > V_{R1}$ )



If  $V_i > V_{R2}$ ,  $V_{D1}$  is positive ( $D_1$  is OFF) &  $V_{D2}$  is also positive ( $D_2$  is ON), so  $V_O = V_{R2}$

If  $V_i < V_{R1}$ ,  $V_{D1}$  is negative ( $D_1$  is ON) &  $V_{D2}$  is also negative ( $D_2$  is OFF), so  $V_O = V_{R1}$

If  $V_{R1} < V_i < V_{R2}$ ,  $V_{D1}$  is positive ( $D_1$  is OFF) &  $V_{D2}$  is negative ( $D_2$  is OFF),

so  $V_O = V_i$

**Transfer characteristics:**

It is a plot of output voltage as a function of input voltage.

If  $V_i > V_{R2}$ , Then  $V_O = V_{R2}$  so slope of transfer characteristics curve is zero

If  $V_i < V_{R1}$ , Then  $V_O = V_{R1}$  so slope of transfer characteristics curve is zero.

## CLIPPERS

## UNIT-2

If  $V_{R1} < V_i < V_{R2}$ , Then  $V_O = V_i$  so slope of transfer characteristics curve is one.

